



### Försättsblad Prov Original

Kurskod	ET027G	Provkod	T101	Tentamensdatum	2018 - 06 - 11
Kursnamn	Elektroteknik GR (B), Kraftelektronik				
Provnamn	Skriftlig tentamen				
Ort	Sundsvall				
Termin	V18				
Ämne	Elektroteknik				



**Re-examination in Power Electronics (ET027G)**

**Date and Time: 11<sup>th</sup> June 2018 and 8:00 – 12:00 (alt 09:00 – 13:00)**

**Responsible Teacher: Kent Bertilsson, Tel: 010-142 8915, Email: [Kent.Bertilsson@miun.se](mailto:Kent.Bertilsson@miun.se)**

---

**Permitted aids:** *Scientific Calculator, Eng-Swe Lexicon, Formula collection attached*

**Maximum points:** 46p

**Preliminary grading levels:** A  $\geq 42$ p, B  $\geq 38$ p, C  $\geq 34$ p, D  $\geq 29$ p, E  $\geq 23$ p; F < 23p

- Start every new exercise on a blank paper
- Written text and figures should be clearly drawn and graphs in scale with labeled axes.
- The solution should be logically written and used equations should be motivated.
- The calculations should be sufficiently complete to show how the final result was obtained.
- Each task must be concluded with a clearly written answer (underline the obtained answer).
- If you don't get an answer in one part of the exercise that is required for continuing calculations in later sections you can calculate with variables only.

Good Luck

Kent

---

1) Short questions.


- What is the advantages and disadvantages of linear and switched mode converters (2p)
  - Order the switching devices MOSFETs, Bipolar transistors, IGBT and Thyristors in each of the three categories 1) power rating, 2) switching speed and 3) drive complexity. (6p)
  - Describe the differences in harmonics between a square wave modulated and a pulse width modulated inverter (2p)
- Tot 10p

2) Assume a constant current of 10A in diode rectifier is switched with duty cycle of 60% with a forward voltage drop of 0.9V.

- How much is the losses reduced replacing this with a synchronous rectifier with a MOSFET with  $r_{dson}=10\text{m}\Omega$  (3p)
  - How much is the efficiency increased assuming this is used in a flyback converter with  $P_{out}=200\text{W}$  and previous efficiency of 91%. (3p)
- Tot 6p




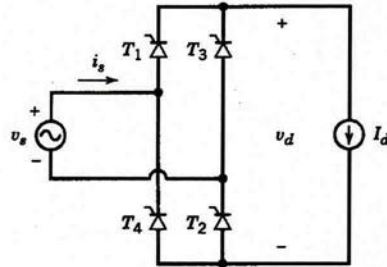- 3) The thyristor based inverter below drives a large inductor that can be treated as a current source. The input is fed by the Swedish grid with 50Hz AC voltage with  $V_{RMS}=230V$ . The firing angle of the thyristors is  $30^\circ$ .



- Draw the wave forms for the input voltage, load voltage and the source current (3p)
  - Calculate the average load voltage,  $V_d$  (1p)
  - Calculate the displacements, distortion and total power factor for the circuit (2p)
- (Tot 6p)
- 4) The converter below has  $V_{in}=200V$ , Duty cycle=40% is working in continuous conduction mode. The primary winding have 100 turns and the secondary 10 turns and the converter is loaded with  $10\Omega$ .
- What type of converter is shown (1p)
  - Calculate the output voltage,  $V_o$  (1p)
  - What is the functionality of the transistor in the right circle (1p)
  - What is the functionality of the circuit elements in the left oval (1p)
  - Sketch the waveforms for the primary switch current,  $I_{Sw}$ , Rectifier current,  $I_{Rect}$ , Switch voltage,  $V_{Sw}$ , The amplitude for the voltages should be clearly shown. The mean currents should be correct and clearly visible. (6p)


Tot 10p

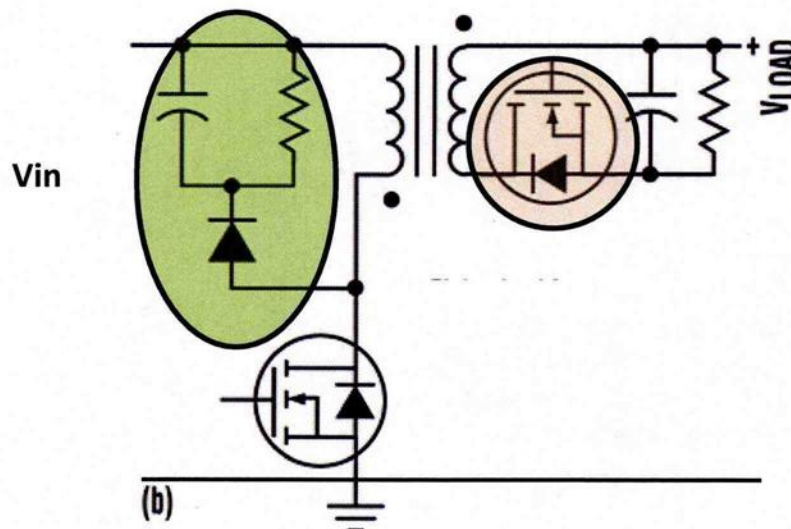

(b)




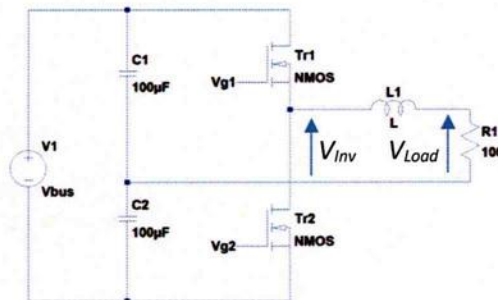- 5) A single phase inverter according to the figure below is driving a 100Ohm load. A triangular and sinusoidal shown waveform (1<sup>st</sup> graph) are used to generate the switching pattern for the two switches (2<sup>nd</sup> and 3<sup>rd</sup> graph). The 4<sup>th</sup> graph shows the output from the inverter before and after the inductor and the resulting current is shown in the 5<sup>th</sup> graph.



- Determine the switching frequency and the inverter output frequency (1p)
- Determine the amplitude and frequency modulation ratios,  $m_A$  and  $m_f$  (1p)
- Determine the bus voltage,  $V_{Bus}$  (1p)
- Determine the size of the inductor L1 used. (3p)
- A single phase synchronous motor marked 60Hz, 1400rpm is connected to the driver. Determine the motor speed in rpm. (2p)

Tot 8p

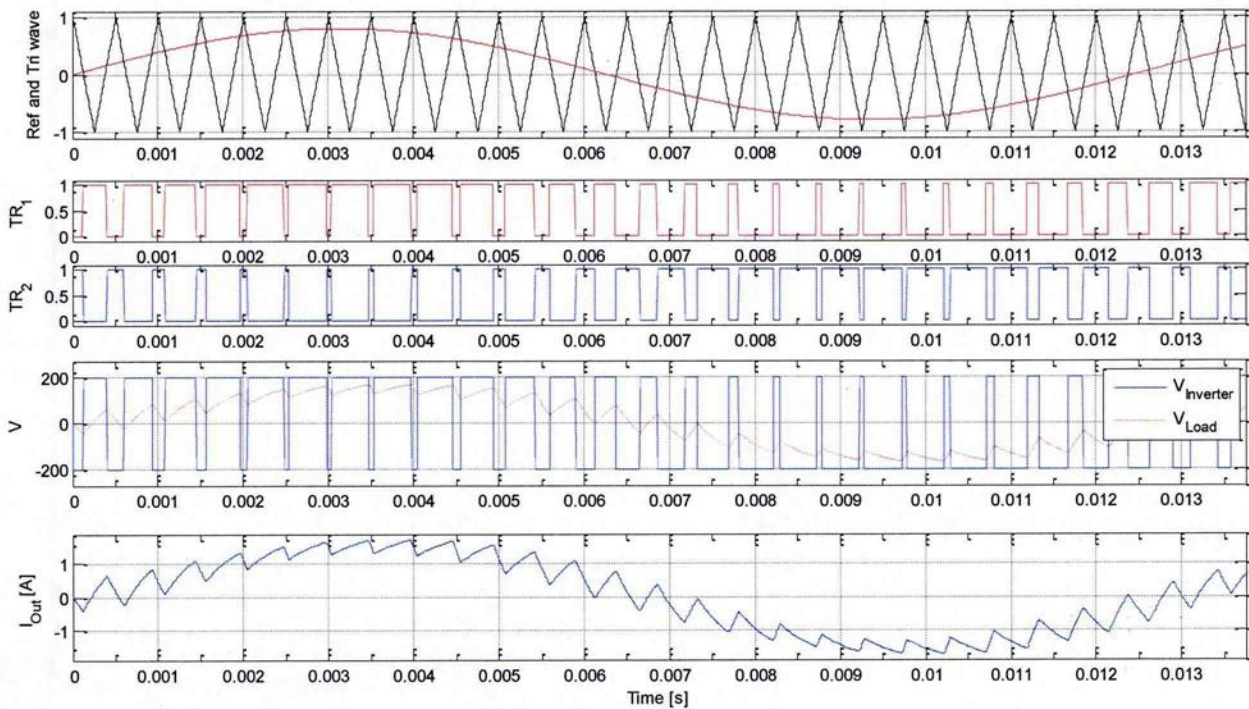



6) A transistor is dissipating 10W in losses under steady state. According to datasheets for the transformer and heatsink the thermal resistances are  $R_{Th\ junction-case} = 0.5K/W$ ,  $R_{Th\ case-sink} = 1.5K/W$ ,  $R_{Th\ sink-ambient} = 3K/W$ . The ambient is expected to be at most 30°C.

- a. Draw a thermal schematic of the situation. (2p)
- b. What is the highest junction temperature of the transistor (2p)

Under a surge event the losses can reach 1000W for 10us. Assuming that it is only the chip temperature that response to the surge and the corresponding thermal capacitance is 0.01 J/K.

- c. Estimate the temperature the chip reach during such surge (2p)

Tot 6p