



Försättsblad Prov Original

Kurskod	Provkod	Tentamensdatum
E T 0 2 7 G	T 1 0 1	2 0 1 9 - 0 3 - 1 8
Kursnamn	Elektroteknik GR (B), Kraftelektronik	
Provnamn	Tentamen - Sundsvall	
Ort	Sundsvall	
Termin	VT2019	
Ämne	Elektroteknik	

Power Electronics Exam (ET027G)

Date and Time: 18th March 2019 and 8:00 – 12:00

Responsible Teacher: Sobhi Barg, Tel: 010-142 79 91, Email: sobhi.barg@miun.se

Maximum points: 55

Preliminary grades: A \geq 53pt, B \geq 48pt, C \geq 43pt, D \geq 38pt, E \geq 33pt, F $<$ 28pt

Introduction:


- The exam includes two answer sheets, please return them with your answer sheets.
- The exam includes 4 parts, which are completely separate.
- The first part contains Yes or No type Questions. Full mark will be given for correct answer and zero for incorrect answer.
- The second part is a problem about the full-bridge rectifier.
- The third part is a problem about the boost converter.
- The fourth part is a problem about the three phase inverter.
- Each numerical result has to be preceded by full and clear development of the analytical expression.
- The exam includes a formula sheet.
- The use of scientific calculator is allowed.
- English to Swedish dictionary is allowed.

I. Part One (15 pts)

Complete the following sentences by Yes or No


- In switching mode power supply, the transistor is operated in the active region:
- The power Bjt transistor has better switching capability than the power MOSFET:
- The conduction loss depends on the switching frequency:
- At high frequency, the switching loss are higher than the conduction loss:
- The power MOSFET is a current controlled device:
- The maximum output voltage of the full bridge diode rectifier is 207 V:
- The average output voltage of the three phase diode rectifier is
- The AC line input inductance increases the average output voltage of the rectifier:
- The harmonics currents are part of the active power:
- The output voltage of a buck converter is dependent on the load current:
- In buck converter, the inductance is proportional to the output current ripple:
- For DC-DC converters, the inductance for DCM is bigger than that for CCM :
- In flyback converter, the magnetic core operates in the first and third quadrant:
- The Mosfet voltage stress in boost converter is higher than that in flyback:
- The ZVS can be realized during the turn-off:

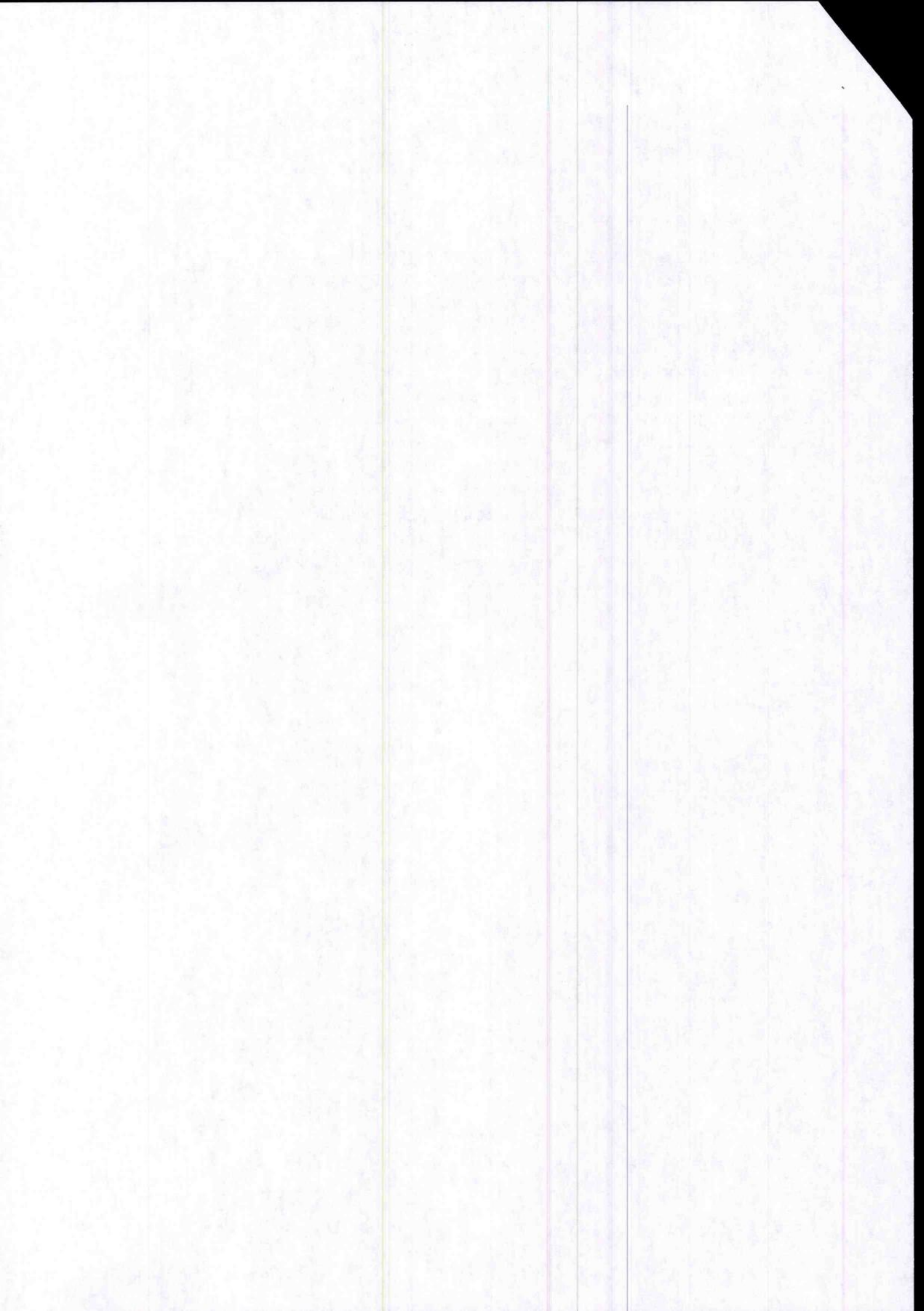Note: Please include this page with your exam answer sheet.



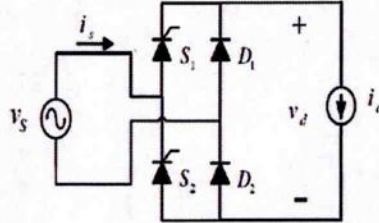II. Part Two (16pts)

Consider the single phase semi-controlled rectifier below. V_s is the AC line voltage $V_s=230$ V, $f=50$ Hz.




- 1- Determine the on-state and off-state conditions of each semi-conductor components in the circuit. (1pt)
- 2- Draw in the same figure, V_s , I_s , V_d for the firing angle $\alpha=45^\circ$, 90° . (1pt)
- 3- In the same figure but in different x-axis draw, the current and the voltage across each components (use different colors). (1pt)
- 4- Determine the expression of the average output voltage V_d and calculate its value for the different firing angles. (2pt)
- 5- Suppose that V_{dc} is the average output voltage when $\alpha=0^\circ$. Calculate the firing angle that gives $V_d=0.5 * V_{dc}$. (2pt)

Suppose that you have a dc voltage source ($V_c= 60$ V)in series with the high inductive load (i_d).

- 6- Draw the new circuit. (1pt)
- 7- What is the average output voltage when the firing angle is equal to 5° (suppose that the triggering pulse is very short (some nano-second)). (2pt)
- 8- Determine the minimum firing angle to get an input voltage higher than V_c . (3pt)
- 9- Determine the firing angle to get an average output voltage V_d 30% higher than V_c . (3pt)

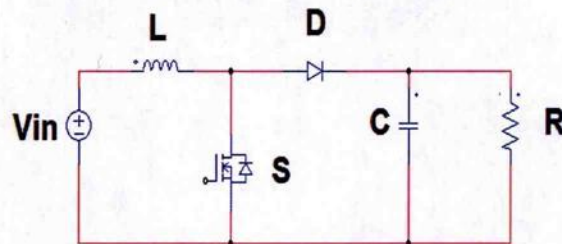III. Part Three (16 pts)

Consider the circuit of a boost converter below. We would like to operate the converter in CCM. $V_{in}=2.3-8$ V, $V_o=12$ V, $f=200$ kHz, $P_o=3.6$ W, $\eta=90$



- 1- Explain the operation of this converter and draw the equivalent circuit for the two cases. (2pt)
 - The switch S is on.
 - The switch S is off.
- 2- Determine the minimum and maximum duty cycle D to get the required output voltage. (2pt)
- 3- Demonstrate that the expression of the output current ripple as function of V_o , D, L and f is equal to: (1pt)

$$\Delta I_o = \frac{V_o D(1 - D)}{Lf}$$

- 4- Calculate $\frac{\Delta I_o}{dD} = 0$ and determine the critical duty cycle for which the current ripple is maximum. (3pt)
- 5- Calculate the critical input voltage that leads to the maximum output current ripple. (2pt)
- 6- Determine the required inductance to get an output current ripple equal to 20% the output DC current at the critical duty cycle. (2pt)
- 7- For the calculated inductance determine the minimum output current ripple that can be achieved. (2pt)
- 8- For $D=0.5$, the calculated inductance and the given frequency, sketch in the same figure: the input voltage, the switch voltage V_{ds} in the first x-axis. In the second x-axis, draw the output current and the switch current. (2pt)

